

Name:
Currents & Circuits- Problem Packet

Period:

Date:

1. A $4.0\ \Omega$ resistor is connected to a $6.0\ \text{V}$ battery. What is the current in the circuit?

2. A $90.0\ \text{V}$ battery does $2.7\ \text{J}$ of work in transferring some charge during a 2.0 second period.
 - a. Calculate the amount of charge transferred.

 - b. Calculate the current flow.

 - c. Calculate the power.

3. An iron is rated at $1680\ \text{W}$ and is connected to a $120\ \text{V}$ outlet.
 - a. Calculate the current that the iron draws.

 - b. Calculate the energy that is consumed by the iron in one hour.

4. A $1.5\ \text{V}$ dry cell is connected to a $4500\ \Omega$ resistor. Calculate the current in this circuit.

5. A $60.0\ \text{W}$ light bulb is connected to a $120\ \text{V}$ outlet.
 - a. Calculate the current flowing through the bulb.

 - b. What is the resistance of the bulb?

6. Eighty percent of the energy used by a sunlamp is converted into heat. When the sunlamp is plugged into a 120 V outlet, it draws 2.0 A. How much thermal energy is released by this lamp in 30 minutes?
7. A transistor radio operates by means of a 9.0 V battery that supplies it with 50 mA (0.0500 A) current.
- If the cost of the battery is \$0.90 and it lasts for 300 hours, what is the cost per kWh to operate the radio in this manner?
 - The same radio, by means of a converter, is plugged into a household circuit by a homeowner who pays \$0.08 per kWh. What does it now cost to operate the radio for 300 h?
8. A 20.0 Ω resistor and a 30.0 Ω resistor are connected in series and placed across a 120 V potential difference.
- Draw a quick sketch of this circuit.
 - What is the equivalent resistance of the circuit?
 - What is the current in the circuit?
 - What is the voltage drop across each resistor?
 - What is the voltage drop across the two resistors together?

9. Three resistors of $3.0\text{ k}\Omega$, $5.0\text{ k}\Omega$, and $4.0\text{ k}\Omega$ are connected in series across a 12 V battery.
- Draw a quick sketch of this circuit.
 - What is the equivalent resistance of the circuit?
 - What is the current through the resistors?
 - What is the voltage drop across each resistor?
 - Find the total voltage drop across the three resistors.
10. A $120\ \Omega$ resistor, a $60\ \Omega$ resistor, and a $40\ \Omega$ resistor are connected in parallel and placed across a 12 V battery.
- Draw a quick sketch of this circuit.
 - What is the equivalent resistance of the parallel circuit?
 - What is the current through the entire circuit?
 - What is the current through each branch of the circuit?

11. Three $15\ \Omega$ resistors are connected in parallel and placed across a 30 V battery.

- a. Draw a quick sketch of the circuit.

- b. What is the equivalent resistance of the parallel circuit?

- c. What is the current through the entire circuit?

- d. What is the current through each branch of the circuit?




12. Suppose one of the $15.0\ \Omega$ resistors in problem #11 is replaced by a $10.0\ \Omega$ resistor.

- a. Does the equivalent resistance change? If so, how?

- b. Does the amount of current through the entire circuit change? If so, in what way?

- c. Does the amount of current through the other $15.0\ \Omega$ resistors change? If so, in what way?




13

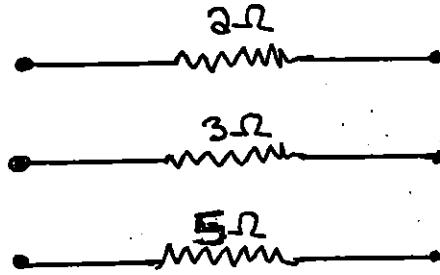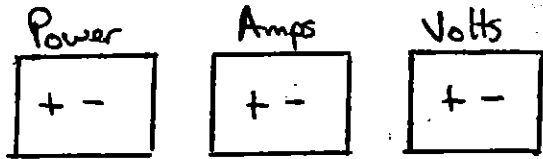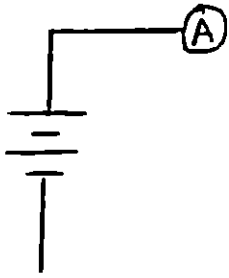

Resistor R_1 is connected in series with the parallel combination of R_2 and R_3 . The ammeter measures current out of the power supply and a voltmeter is reading the voltage across R_1 . Complete the schematic diagram and complete the chart below according to the circuit.

Resistor	Resistance (ohms)	Current (amps)	Voltage (Volts)	Power (Watts)
1	2 Ω			
2	3 Ω			
3	5 Ω			
Total			31 V	

14

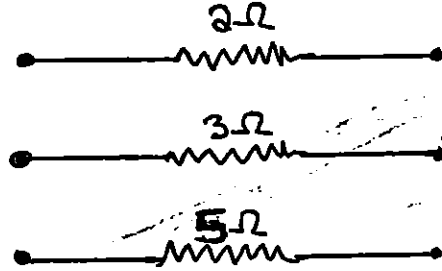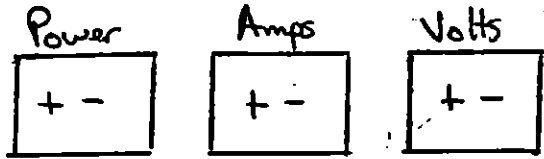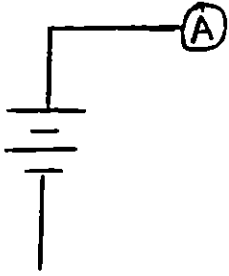

Resistor R_1 is connected in series with R_2 and the combination is parallel with R_3 . The ampmeter measures current out of the power supply and a voltmeter is reading the voltage across R_3 . Complete the schematic diagram and complete the chart below according to the circuit.

Resistor	Resistance (ohms)	Current (amps)	Voltage (Volts)	Power (Watts)
1	2 Ω			
2	3 Ω			
3	5 Ω			
Total			31 V	