



1. A 4.0Ω resistor is connected to a 6.0 V battery. What is the current in the circuit?

$$R = \frac{V}{I}$$

$$I = \frac{V}{R} = \frac{6 \text{ V}}{4 \Omega} = \boxed{1.5 \text{ A}}$$

$$\frac{\text{V/c}}{\text{A}\cdot\text{s}/\text{c}} = \text{c/s} = \text{A}$$

2. A 90.0 V battery does 2.7 J of work in transferring some charge during a 2.0 second period.

- a. Calculate the amount of charge transferred.

$$V = \frac{PE}{Q}$$

$$Q = \frac{PE}{V} = \frac{2.7 \text{ J}}{90 \text{ V}} = \boxed{.03 \text{ C}}$$

$$\frac{\text{J}}{\text{A}\cdot\text{c}} = \text{C}$$

- b. Calculate the current flow.

$$I = \frac{Q}{t} = \frac{.03 \text{ C}}{2 \text{ sec}} = \boxed{.015 \text{ A}}$$

$$\text{c/s} = \text{A}$$

- c. Calculate the power.

$$P = I \cdot V = .015 \text{ A} \times 90 \text{ V} = \boxed{1.35 \text{ Watts}}$$

$$\frac{\text{c}}{\text{s}} \times \frac{\text{J}}{\text{c}} = \frac{\text{J}}{\text{s}} = \text{Watts}$$

3. An iron is rated at 1680 W and is connected to a 120 V outlet.

- a. Calculate the current that the iron draws.

$$P = I \cdot V \quad I = \frac{P}{V} = \frac{1680 \text{ Watts}}{120 \text{ V}} = \boxed{14 \text{ A}}$$

$$\frac{\text{J/s}}{\text{A}\cdot\text{c}} = \text{c/s} = \text{A}$$

- b. Calculate the energy that is consumed by the iron in one hour.

$$\text{Energy} = P \times \text{time} = 1680 \text{ Watts} \times 3600 \text{ sec} = \text{or}$$

$$6048000 \text{ J} \left(\frac{1 \text{ kWh}}{3.6 \times 10^6 \text{ J}} \right) = \boxed{1.68 \text{ kWh}} \quad 6048000 \text{ J} = \boxed{6048 \text{ kJ}}$$

$$1680 \text{ Watts} = 1.68 \text{ kWh/hr} = \boxed{1.68 \text{ kWh}}$$

$$1 \text{ hr} = 3600 \text{ s}$$


4. A 1.5 V dry cell is connected to a 4500Ω resistor. Calculate the current in this circuit.

$$R = \frac{V}{I} \quad I = \frac{V}{R} = \frac{1.5 \text{ V}}{4500 \Omega} = \boxed{3.33 \times 10^{-4} \text{ A}}$$

5. A 60.0 W light bulb is connected to a 120 V outlet.

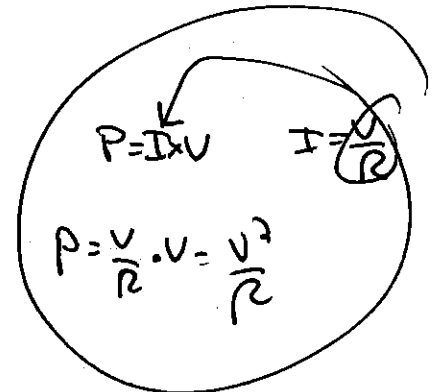- a. Calculate the current flowing through the bulb.

$$P = I \cdot V \quad I = \frac{P}{V} = \frac{60 \text{ W}}{120 \text{ V}} = \boxed{.5 \text{ A}}$$



- b. What is the resistance of the bulb?

$$\frac{\text{J/c}}{\text{c/s}} = \frac{\text{J}\cdot\text{s}}{\text{c}^2} = \Omega \quad R = \frac{V}{I} = \frac{120 \text{ V}}{.5 \text{ A}} = \boxed{240 \Omega}$$

$$P = \frac{V^2}{R} \quad R = \frac{V^2}{P} = \frac{(120 \text{ V})^2}{60 \text{ W}} = \boxed{240 \Omega} \quad \frac{(\text{J/c})^2}{\text{J/s}} = \frac{\text{J}^2/\text{c}^2}{\text{J/s}} = \frac{\text{J}\cdot\text{s}}{\text{c}^2} = \Omega$$

6. Eighty percent of the energy used by a sunlamp is converted into heat. When the sunlamp is plugged into a 120 V outlet, it draws 2.0 A. How much thermal energy is released by this lamp in 30 minutes?

$$30 \text{ min} = 1800 \text{ s}$$

$$\text{Energy} = P \times \text{time}$$

$$P = I \times V$$

$$\text{Energy} = I \times V \times \text{time} = 2 \text{ A} \times 120 \text{ V} \times 1800 \text{ s} = 432,000 \text{ J} \times .8 = 345,600 \text{ J}$$

$$\frac{\text{J}}{\text{s}} = \frac{\text{kJ}}{\text{h}} \times \frac{\text{h}}{\text{s}}$$

$$345,600 \text{ J} \left(\frac{1 \text{ kWh}}{3.6 \times 10^6 \text{ J}} \right) = \boxed{.096 \text{ kWh}}$$

7. A transistor radio operates by means of a 9.0 V battery that supplies it with 50 mA (0.0500 A) current.

- a. If the cost of the battery is \$0.90 and it lasts for 300 hours, what is the cost per kWh to operate the radio in this manner?

$$P = I \times V = (.05)(9) = .45 \text{ W} = .00045 \text{ kW} \times 300 \text{ h} = \boxed{.135 \text{ kWh}}$$

$$300 \text{ h} \times 3600 \text{ s/h} = 1,080,000 \text{ sec}$$

$$\text{Energy} = I \times V \times \text{time} = (.05 \text{ A})(9 \text{ V})(1,080,000 \text{ sec}) = 486,000 \text{ J} \left(\frac{1 \text{ kWh}}{3.6 \times 10^6 \text{ J}} \right) = \boxed{.135 \text{ kWh}}$$


$$\frac{\$.90}{.135 \text{ kWh}} = \boxed{\$ 6.67/\text{kWh}}$$

- b. The same radio, by means of a converter, is plugged into a household circuit by a homeowner who pays \$0.08 per kWh. What does it now cost to operate the radio for 300 h?

$$P = I \times V = .45 \text{ watts} = .00045 \text{ kW} \times 300 \text{ h} = .135 \text{ kWh} \times \$.08/\text{kWh} = \boxed{\$.0108}$$

8. A 20.0 Ω resistor and a 30.0 Ω resistor are connected in series and placed across a 120 V potential difference.

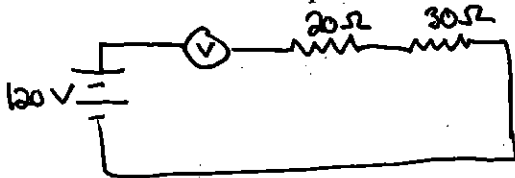- a. Draw a quick sketch of this circuit.



- b. What is the equivalent resistance of the circuit?

$$R_T = R_1 + R_2 = 20 \Omega + 30 \Omega = \boxed{50 \Omega}$$

- c. What is the current in the circuit?

$$I = \frac{V}{R} = \frac{120 \text{ V}}{50 \Omega} = \boxed{2.4 \text{ A}}$$

- d. What is the voltage drop across each resistor?

$$\overset{20 \Omega}{V} = I \times R = (2.4 \text{ A}) \times 20 \Omega = \boxed{48 \text{ V}}$$

$$\overset{30 \Omega}{V} = I \times R = 2.4 \text{ A} \times 30 \Omega = \boxed{72 \text{ V}}$$


- e. What is the voltage drop across the two resistors together?

$$\boxed{120 \text{ V}}$$

$$V_T = V_1 + V_2 = 48 \text{ V} + 72 \text{ V} = \boxed{120 \text{ V}}$$

9. Three resistors of $3.0 \text{ k}\Omega$, $5.0 \text{ k}\Omega$, and $4.0 \text{ k}\Omega$ are connected in series across a 12 V battery.

a. Draw a quick sketch of this circuit.

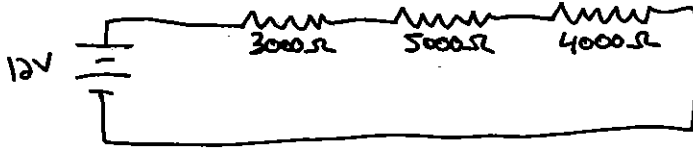

b. What is the equivalent resistance of the circuit?

$$R_T = R_A + R_B + R_C = 3000\Omega + 5000\Omega + 4000\Omega = \boxed{12000\Omega}$$

c. What is the current through the resistors?

$$I = \frac{V}{R} = \frac{12\text{V}}{12000\Omega} = \boxed{.001 \text{ A}}$$

d. What is the voltage drop across each resistor?

$$V_1 = I_1 \cdot R_1 = .001 \text{ A} \cdot 3000\Omega = 3\text{V}$$

$$V_2 = I_2 \cdot R_2 = .001 \text{ A} \cdot 5000\Omega = 5\text{V}$$


$$V_3 = I_3 \cdot R_3 = .001 \text{ A} \cdot 4000\Omega = 4\text{V}$$

e. Find the total voltage drop across the three resistors.

$$\boxed{12\text{V}} \quad V_T = V_1 + V_2 + V_3 = 3\text{V} + 5\text{V} + 4\text{V} = \boxed{12\text{V}}$$

10. A 120Ω resistor, a 60Ω resistor, and a 40Ω resistor are connected in parallel and placed across a 12 V battery.

a. Draw a quick sketch of this circuit.

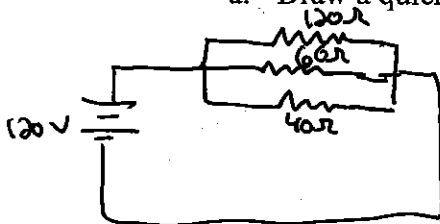

b. What is the equivalent resistance of the parallel circuit?

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{120} + \frac{1}{60} + \frac{1}{40} = \frac{1}{120} + \frac{2}{120} + \frac{3}{120} = \frac{6}{120} = \frac{1}{20}$$

$$\frac{1}{R_T} = \frac{1}{20} \quad \boxed{R_T = 20\Omega}$$

c. What is the current through the entire circuit?

$$I = \frac{V}{R} = \frac{12\text{V}}{20\Omega} = \boxed{.6 \text{ A}}$$

d. What is the current through each branch of the circuit?

$$I_1 = \frac{V_1}{R_1} = \frac{12\text{V}}{120\Omega} = \boxed{.1 \text{ A}}$$


$$I_2 = \frac{V_2}{R_2} = \frac{12\text{V}}{60\Omega} = \boxed{.2 \text{ A}}$$

$$I_3 = \frac{V_3}{R_3} = \frac{12\text{V}}{40\Omega} = \boxed{.3 \text{ A}}$$

$$I_T = I_1 + I_2 + I_3 = .1 + .2 + .3 = \boxed{.6 \text{ A}}$$

11. Three $15\ \Omega$ resistors are connected in parallel and placed across a $30\ \text{V}$ battery.

a. Draw a quick sketch of the circuit.

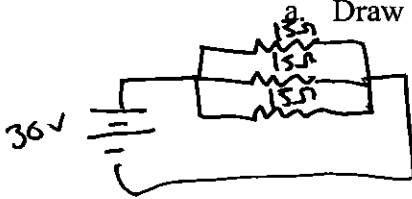

b. What is the equivalent resistance of the parallel circuit?

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \frac{1}{R_T} = \frac{1}{15\ \Omega} + \frac{1}{15\ \Omega} + \frac{1}{15\ \Omega} = \frac{3}{15\ \Omega} \quad \boxed{R_T = 5\ \Omega}$$

c. What is the current through the entire circuit?

$$I = \frac{V}{R} = \frac{30\ \text{V}}{5\ \Omega} = \boxed{6\ \text{A}}$$

d. What is the current through each branch of the circuit?

$$I_1 = \frac{V_1}{R_1} = \frac{30\ \text{V}}{15\ \Omega} = \boxed{2\ \text{A}} \quad \text{- each one is the same} \quad \begin{matrix} I_T = I_1 + I_2 + I_3 = \\ 2\ \text{A} + 2\ \text{A} + 2\ \text{A} = \end{matrix} \boxed{6\ \text{A}}$$

12. Suppose one of the $15.0\ \Omega$ resistors in problem #11 is replaced by a $10.0\ \Omega$ resistor.

a. Does the equivalent resistance change? If so, how?

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{15} + \frac{1}{15} + \frac{1}{10} = \frac{2}{30} + \frac{2}{30} + \frac{3}{30} = \frac{7}{30} = \frac{1}{R_T} \quad \boxed{R_T = 4.28\ \Omega}$$

b. Does the amount of current through the entire circuit change? If so, in what way?

$$I = \frac{V}{R} = \frac{30\ \text{V}}{4.28\ \Omega} = \boxed{7\ \text{A}} \quad \text{Yes} \rightarrow$$

c. Does the amount of current through the other $15.0\ \Omega$ resistors change? If so, in what way?



$$I_1 = \frac{V_1}{R_1} = \frac{30\ \text{V}}{15\ \Omega} = 2\ \text{A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{30\ \text{V}}{15\ \Omega} = 2\ \text{A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{30\ \text{V}}{10\ \Omega} = 3\ \text{A}$$

$$I_T = I_1 + I_2 + I_3$$
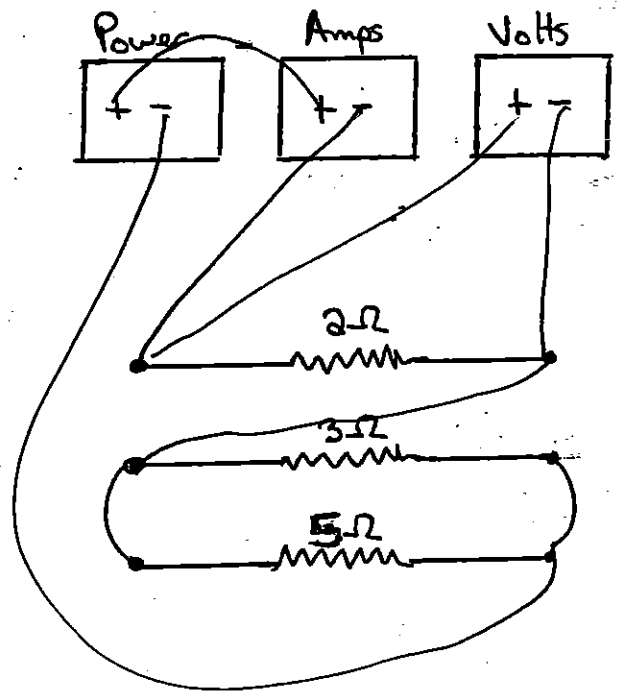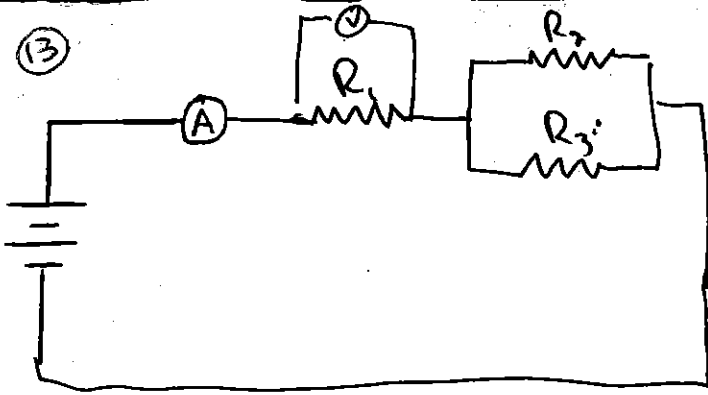
$$I_T = 2 + 2 + 3 = \boxed{7\ \text{A}}$$



Resistor R_1 is connected in series with the parallel combination of R_2 and R_3 . The ampmeter measures current out of the power supply and a voltmeter is reading the voltage across R_1 . Complete the schematic diagram and complete the chart below according to the circuit.

Resistor	Resistance (ohms)	Current (amps)	Voltage (Volts)	Power (Watts)
1	$2\ \Omega$	⑤ 8A	⑥ 16V	⑩ 128 Watts
2	$3\ \Omega$	⑨ 5A	⑧ 15V	⑪ 75 Watts
3	$5\ \Omega$	⑬ 3A	⑧ 15V	⑫ 45 Watts
Total	⑭ $3.875\ \Omega$	③ 8A	31V	④ 248 Watts

① $\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{3} + \frac{1}{5} = \frac{5}{15} + \frac{3}{15}$

$R_{23} = \frac{15}{8} = 1.875\ \Omega$

② $R_T = R_1 + R_{23} = 2\ \Omega + 1.875\ \Omega = 3.875\ \Omega$

③ $I_T = \frac{V_T}{R_T} = \frac{31V}{3.875\ \Omega} = 8A$

④ $P_T = I_T \times V_T = 8A \times 31V = 248\ \text{Watts}$

⑤ Series Circ $I_T = I_1 = I_{23} = 8A$

⑥ $V_1 = I_1 \times R_1 = 8A \times 2\ \Omega = 16V$

⑦ $P_1 = I_1 \times V_1 = 8A \times 16V = 128\ \text{Watts}$

⑧ ~~Series~~ Series Circuit $V_T = V_1 + V_{23}$
 $31V = 16V + V_{23}$
 $V_{23} = 15V$

Parallel Circ.
 $V_{23} = V_2 = V_3 = 15V$



⑨ $I_2 = \frac{V_2}{R_2} = \frac{15V}{3\ \Omega} = 5A$

⑪ $P_2 = I_2 \times V_2 = 5A \times 15V = 75W$

⑩ $I_3 = \frac{V_3}{R_3} = \frac{15V}{5\ \Omega} = 3A$

⑫ $P_3 = I_3 \times V_3 = 3A \times 15V = 45W$

14

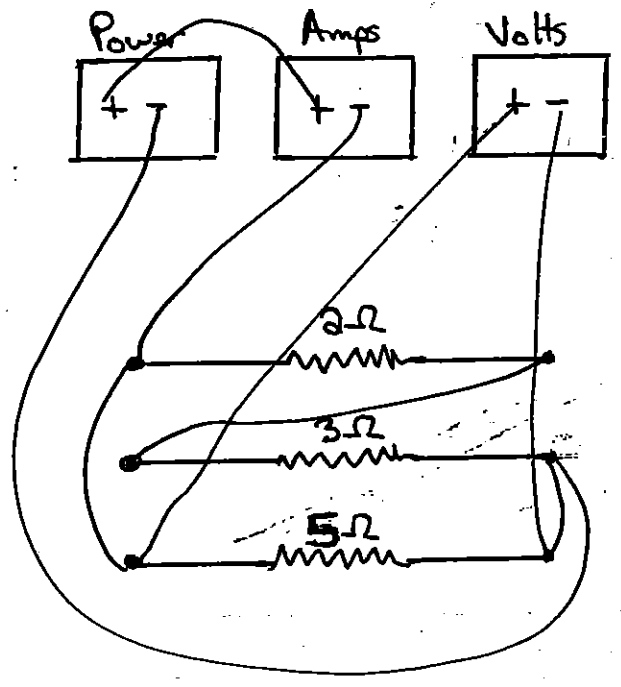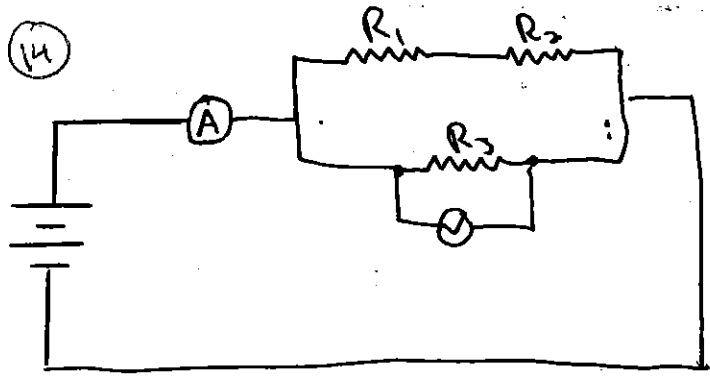

Resistor R_1 is connected in series with R_2 and the combination is parallel with R_3 . The ammeter measures current out of the power supply and a voltmeter is reading the voltage across R_3 . Complete the schematic diagram and complete the chart below according to the circuit.

Resistor	Resistance (ohms)	Current (amps)	Voltage (Volts)	Power (Watts)
1	$2\ \Omega$	⑦ $6.2\ A$	⑧ $12.4\ V$	⑩ $76.88\ \text{Watts}$
2	$3\ \Omega$	⑦ $6.2\ A$	⑨ $18.6\ V$	⑪ $115.32\ \text{Watt}$
3	$5\ \Omega$	⑤ $6.2\ A$	④ $31\ V$	⑥ $192.2\ \text{Watts}$
Total	① $2.5\ \Omega$	② $12.4\ A$	$31\ V$	③ $384.4\ \text{Watts}$

① $R_{1/2} = R_1 + R_2 = 2\ \Omega + 3\ \Omega = 5\ \Omega$
 $\frac{1}{R_T} = \frac{1}{R_{1/2}} + \frac{1}{R_3} = \frac{1}{5\ \Omega} + \frac{1}{5\ \Omega} = \frac{2}{5}$
 $R_T = \frac{5}{2} = 2.5\ \Omega$

⑤ $I_3 = \frac{V_3}{R_3} = \frac{31\ V}{5\ \Omega} = 6.2\ A$

⑥ $P_3 = I_3 \times V_3 = 6.2\ A \times 31\ V = 192.2\ \text{Watts}$

⑦ Parallel Circ. $I_T = I_{1/2} + I_3$
 $12.4 = I_{1/2} + 6.2 \quad I_{1/2} = 6.2\ A$

Series Circ $I_{1/2} = I_1 = I_2 = 6.2\ A$

② $I_T = \frac{V_T}{R_T} = \frac{31\ V}{2.5\ \Omega} = 12.4\ A$

⑧ $V_1 = I_1 \times R_1 = 2\ \Omega \times 6.2\ A = 12.4\ V$

⑨ $V_2 = I_2 \times R_2 = 3\ \Omega \times 6.2\ A = 18.6\ V$

③ $P_T = I_T \times V_T = 12.4\ A \times 31\ V = 384.4\ \text{Watts}$

⑩ $P_1 = I_1 \times V_1 = 6.2\ A \times 12.4\ V = 76.88\ \text{Watts}$

⑪ $P_2 = I_2 \times V_2 = 6.2\ A \times 18.6\ V = 115.32\ \text{Watts}$

④ Parallel Circ. $V_T = V_{1/2} = V_3 = 31\ V$